

KATHMANDU UNIVERSITY
End-Semester Examination
August, 2018

Marks Scored:

Level : B.E.
Year : III

Course : EPEG 318
Semester: II

Exam Roll No. :

Time: 30 mins.

F.M. : 10

Registration No.:

Date AUG 20 2018

SECTION "A"

[20 Q × 0.5=10 marks]


Choose the most appropriate answer.

1. The major advantage of a bridge rectifier is that
 - a. Centre tap transformer is not required.
 - b. Peak inverse voltage of each diode is double of that for a full wave rectifier.
 - c. Peak inverse voltage of each diode is half of that for a full wave rectifier.
 - d. The output voltage is smoother.
2. In a three phase half wave rectifier, the output voltage is equal to
 - a. The most positive input phase voltage at any instant.
 - b. The difference of most positive and most negative input phases at any instant.
 - c. The average value of three phases.
 - d. The difference of the two positive phase voltages.
3. As the number of phases in a multiphase rectifier are increased, the output
 - a. Remains the same.
 - b. Becomes smoother.
 - c. Decreases.
 - d. Diodes will require high PIV.
4. A single phase bridge rectifier has a purely resistive load, $R=10\Omega$, the peak supply voltage $V_m=170$ V, and the supply frequency, $f=60$ Hz. The average output of the rectifier if the source inductance is negligible will be
 - a. 113.3 V.
 - b. 54.11 V.
 - c. 27.056V.
 - d. 340V.
5. In a thyristor, holding current is.....
 - a. more than latching current (I_L).
 - b. less than I_L .
 - c. equal to I_L .
 - d. very small.
6. When a thyristor gets turned on, the gate drive
 - a. Should not be removed as it will turn off the SCR.
 - b. May or may not be removed.
 - c. Must be amplified.
 - d. Should be removed in order to avoid increases losses and higher junction temperature.
7. Gate characteristic of a thyristor
 - a. is a straight line passing through the origin.
 - b. is of the type $V_g = a + b \cdot I_g$.
 - c. is a curve between V_g and I_g .
 - d. has a spread between two curves V_g to I_g .

AUG 20 2018

19. In a sinusoidal pulse modulated (SPWM) inverter there are N pulses per half cycle if
 - a. Triangular carrier wave peak coincides with zero of reference sinusoid waveform.
 - b. Triangular carrier wave zero coincides with zero of reference sinusoid waveform.
 - c. Triangular carrier wave peak coincides with peak of reference sinusoid waveform.
 - d. Sinusoid reference wave peak coincides with zero of carrier triangular waveform.

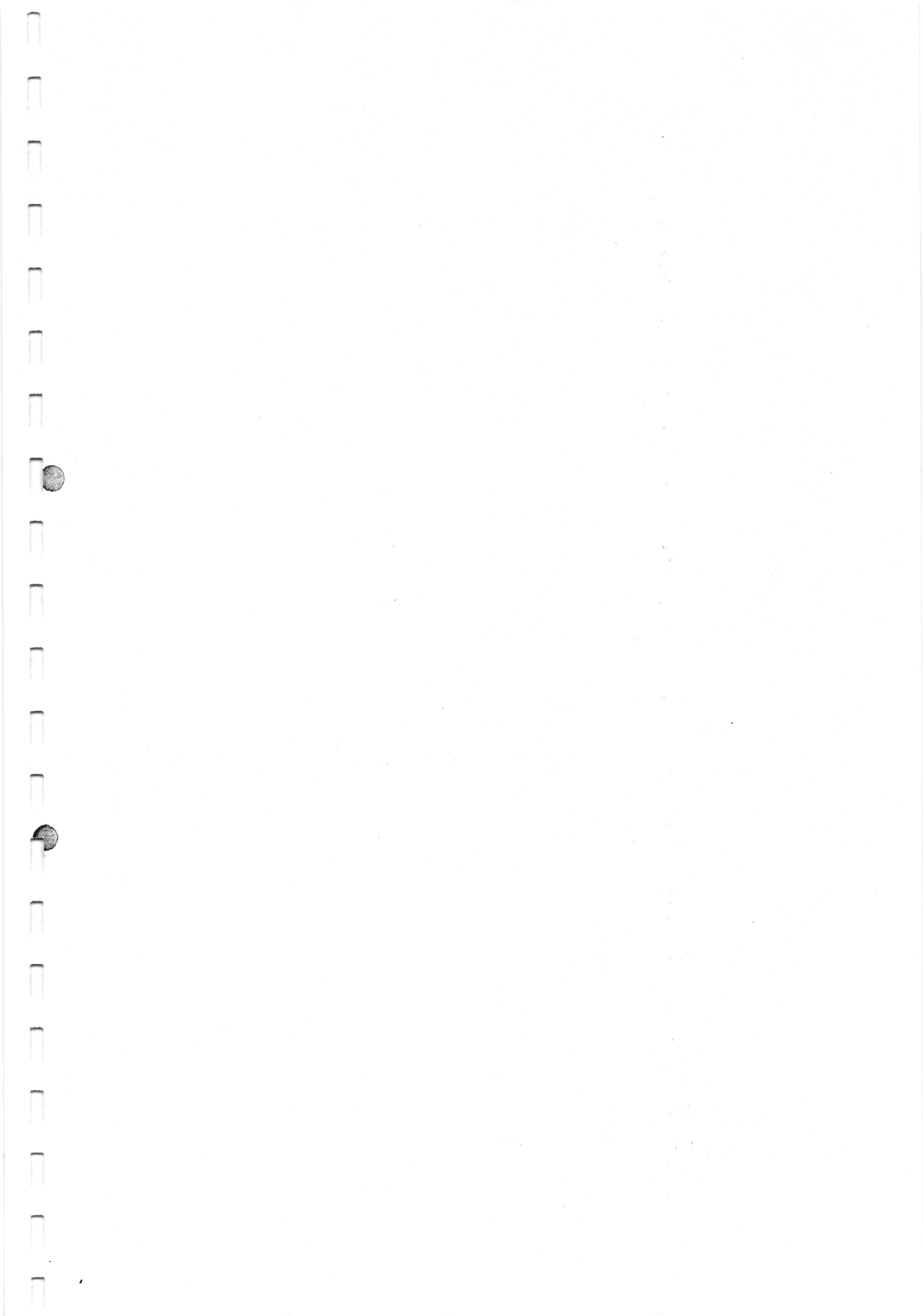20. The cycloconverter requires natural or forced commutation as under
 - a. Natural commutation in both step up and step down cycloconverters.
 - b. Forced commutation in both step up and step down cycloconverters.
 - c. Forced commutation in step up cycloconverters.
 - d. Forced commutation in step down cycloconverters.



KATHMANDU UNIVERSITY
End Semester Examination
August, 2018

AUG 20 2018

Level : B.E.
Year : III
Time : 2 hrs. 30 mins.

Course : EPEG 318
Semester: II
F.M. : 40

SECTION "B"
[5 Q.×8=40 marks]

Attempt ANY FIVE questions. Assume any suitable data if required.

1.
 - a. Describe a three phase to single phase cycloconverter feeding RL load and with output frequency, f_o equal to one fourth of input frequency, f_s . Illustrate your answer by showing one cycle of low frequency of output voltage with clear indication of triggering of various thyristors. [5]
 - b. A single phase half wave controlled rectifier operated from 120V, 60 Hz supply has a purely resistive load, R_L of 10 Ohm and delay angle, $\alpha = \pi/3$. Determine,
 - i. Rectification efficiency.
 - ii. Transformer utilization factor.
 - iii. Peak inverse voltage (PIV) of thyristor. [1+1+1=3]
2.
 - a. Describe a three phase voltage source bridge type inverter using six thyristors and six diodes with 180° conduction mode. Obtain the waveform for a phase voltage, V_{an} for a period of $0 \leq \omega t \ll 2\pi$. [5]
 - b. A step up chopper has input voltage of 220 V and output voltage of 660V. If the non-conducting time of thyristor is $100\mu\text{sec}$. compute the pulse width of output voltage. [3]
3.
 - a. Explain the working principle of a three phase half wave controlled converter with resistive load for a firing angle of, $\alpha = 0^\circ$ and verify that average output voltage, $V_o = \frac{3V_{ml}}{2\pi} * \cos\alpha$, where, V_{ml} = maximum value of line voltage. [5]
 - b. Prove that for a buck-boost converter, output voltage $V_o = V_{in} * [D/(1-D)]$; where V_{in} is the input voltage to the converter and $D = T_{ON} / T$ is the duty cycle of the converter. [3]
4.
 - a. Explain the working principle of a three phase twelve pulse rectifier with necessary waveforms. [4]
 - b. The reverse recovery time of a diode is $t_{rr} = 5\mu\text{s}$, and the rate of fall of the diode current is $di/dt = 80\text{A}/\mu\text{s}$. If the softness factor is $SF = 0.5$, determine a) the storage charge Q_{rr} and b) the peak reverse current I_{RR} . [2+2=4]

5.

- a. A three phase thyristor ac switch with configuration as shown in Figure 1 is used between a three phase 440V, 60Hz supply and a three phase Y-connected load. The load power is 20kW at a power factor of 0.95 lagging. Determine
- Peak load current of thyristors.
 - Average current of thyristor.
 - R.m.s current of thyristor.
 - Peak inverse voltage of thyristor.
 - Firing angles of each thyristors.
- [1+1+1+1+1=5]

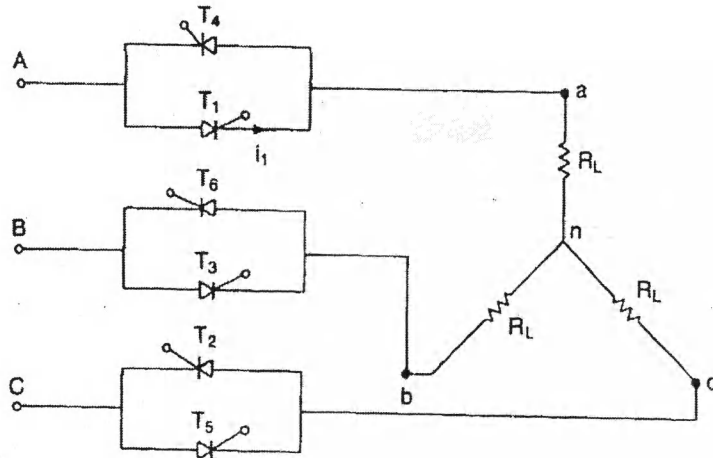


Figure 1. Three phase static ac switch

- b. Plot the output voltage and load current waveform for a single phase full converter with discontinuous current mode of operation assuming firing angle, $\alpha=30^\circ$, extinction angle, $\beta=190^\circ$. [3]
- 6.
- a. Explain the working principle of short break uninterruptible power supply (UPS) and no break UPS with suitable diagram. [2+2=4]
- b. A single phase bridge inverter, fed from 230 V dc is connected to load $R=10 \Omega$ and $L=0.03 \text{ H}$, Determine the power delivered to load considering upto 9th harmonics for a square wave output with inverter operating at frequency of 50 Hz. [4]